

Digital Resistor Sets Operating Power For Laser Driver

By James Horste
ED Online 14977

Derivation of Equations

Equation for Opamp Output Voltage

$$V_{OUT} = V_{REF} \left(-\frac{R_{DS1859}}{R_3} \right) + V_{MD} \left(1 + \frac{R_{DS1859}}{R_3} \right)$$

Rearrange Terms

$$V_{OUT} = V_{MD} + \frac{(V_{MD} - V_{REF}) \cdot R_{DS1859}}{R_3}$$

Substitute 0.2V for Reference Voltage - Modulation Voltage

$$V_{OUT} = V_{MD} - \frac{0.2V \cdot R_{DS1859}}{R_3}$$

Equation for Current through R2

$$I_{R2} = \frac{V_{OUT} - V_{MD}}{R_2}$$

Substitute in equation for OpAmp Output Voltage

$$I_{R2} = \frac{\left(V_{MD} - \frac{0.2V \cdot R_{DS1859}}{R_3} \right) - V_{MD}}{R_2}$$

Modulation voltage terms cancel out

$$I_{R2} = \frac{-0.2V \cdot R_{DS1859}}{R_3 \cdot R_2}$$

Equation for Current through R1

$$I_{R1} = \frac{V_{REF} - V_{MD}}{R_1}$$

Substitute 0.2V for Reference Voltage - Modulation Voltage

$$I_{R1} = \frac{0.2}{R_1}$$

Equation for Current through Photo Diode

$$I_{PD} = I_{R1} + I_{R2}$$

Substitute equations for R1 Current and R2 Current

$$I_{PD} = \frac{0.2}{R_1} - \frac{0.2V \cdot R_{DS1859}}{R_3 \cdot R_2} \quad R_1 = 249 \quad R_2 = 1240 \quad R_3 = 10000$$

$$I_{PD} = 787\mu A \quad DS1859 \text{ Resistance} = 1K \quad I_{PD} = 3.3\mu A \quad DS1859 \text{ Resistance} = 50K$$

Design Procedure

Select Desired Photodiode Min and Max current

$$I_{PDmax} = 800 \cdot 10^{-6} \quad I_{PDmin} = 0$$

$$I_{PDdelta} := I_{PDmax} - I_{PDmin} \quad I_{PDdelta} = 8 \cdot 10^{-4}$$

DS1859 Min and Max Values

$$R_{DS1859max} = 50000 \quad R_{DS1859min} = 1000$$

$$R_{DS1859delta} := R_{DS1859max} - R_{DS1859min} \quad R_{DS1859delta} = 4.9 \cdot 10^4$$

OpAmp Output Voltage Range

$$V_{OUTmax} = 2.0 \quad V_{OUTmin} = 0$$

$$V_{OUTdelta} := V_{OUTmax} - V_{OUTmin} \quad V_{OUTdelta} = 2$$

Modulation Voltage Min and Max

$$V_{MDmin} = 1 \quad V_{MDmax} = 2$$

$$V_{MDdelta} = V_{MDmax} - V_{MDmin} \quad V_{MDdelta} = 1$$

$$R_1 := \frac{0.2}{I_{PDmax}} \quad R_1 = 250$$

$$R_3 := \frac{0.2 \cdot R_{DS1859delta}}{\{V_{OUTdelta} - V_{MDdelta}\}} \quad R_3 = 9.8 \cdot 10^3$$

$$R_2 := 0.2 \cdot \frac{R_{DS1859delta}}{\{I_{PDdelta} R_3\}} \quad R_2 = 1.25 \cdot 10^3$$